



Sequential Logics / Flip-flops

Some Circuits Need Storage

- So far, all of the logic circuits we have talked about have been **combinational**
 - Circuit outputs **only** depend on **current** input values
- But many digital logic circuits we use **need to keep track of past information**


Sequential Circuits

- Some systems need to store information about **past behavior** to know how to react to inputs
 - Generally not storing **everything** that happened, just some key information
 - A vending machine tracks **how much** money has been entered so it knows when it is "enough" to dispense an item
 - Not **which coins or in what order**
- Sometimes just need to store data for later access
 - **Examples:** audio files, digital photos, emails, student grades, bank balances...



Storing a Single Bit


- There are a variety of structures used in digital circuits to store a single bit of information
 - These vary in size, speed, complexity, and behavior
- We focus on one structure: the D flip-flop
 - It has one bit of data input, one bit of data output
 - It also has a "clock" input that controls when the value carried by the input signal is stored into the flip-flop
 - The value held by a flip-flop cannot change until the clock allows it (or power is lost to the system...)
 - The flip-flop's output is always equal to the value it is storing
 - The output updates when a new value is stored into the flip-flop

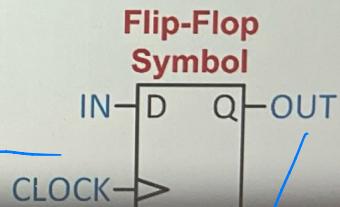

★ current value
"stored"


Clock Signal

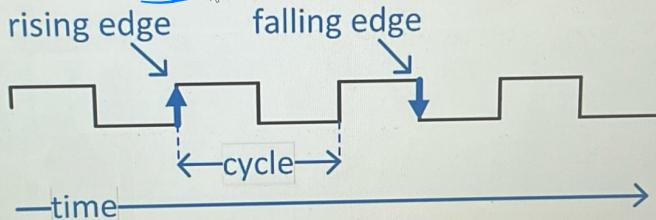- A clock is a special signal that oscillates between 1 and 0 at a specific frequency




Flip-Flop Behavior

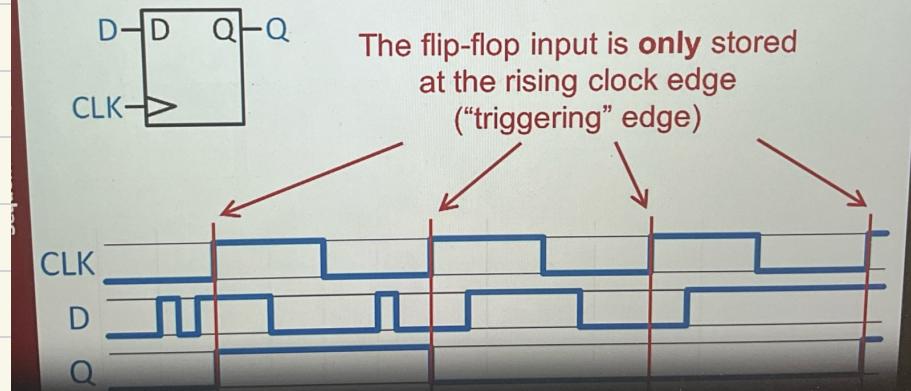- This D flip-flop updates when the clock transitions from 0 to 1 (rising edge)




A Simple Sequential Circuit

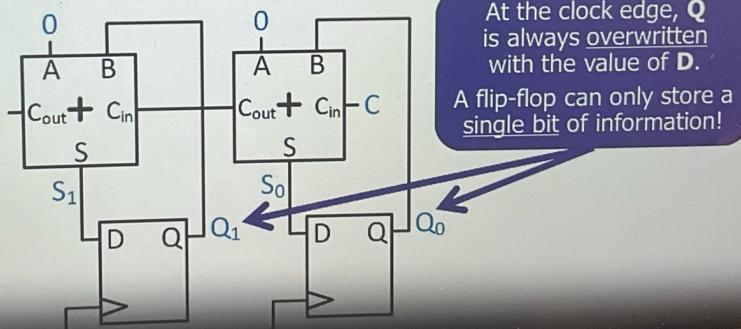- The circuit has a 2-bit adder and 2 flip-flops
 - The flip-flops hold a 2-bit binary number $Q_1 Q_0$
 - The adder implements the arithmetic operation $S_1 S_0 = Q_1 Q_0 + 00_2 + C$
 - At each triggering clock edge, the flip-flops store $S_1 S_0$



Counter Circuit

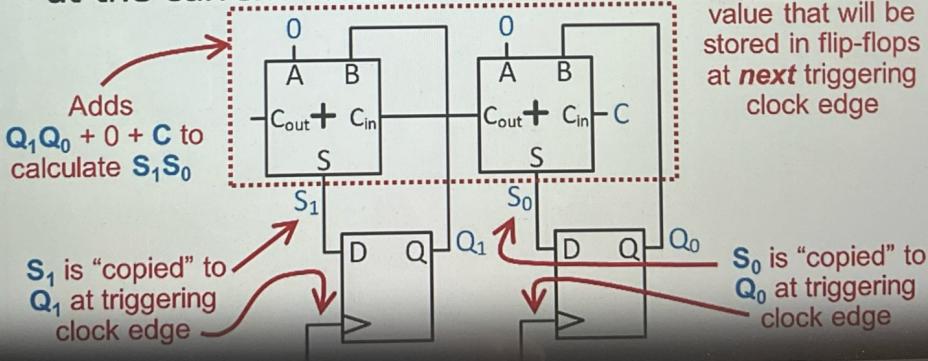- When $C=1$, the circuit counts $00 \rightarrow 01 \rightarrow 10 \rightarrow 11 \rightarrow 00 \rightarrow \dots$
 - The current count value is $Q_1 Q_0$
 - The next count value is $S_1 S_0$
- When $C=0$, the count will hold at the current value




Finite State Machine

- Any practical sequential circuit is a Finite State Machine (FSM)
 - State: current "status" → the contents of the flip-flops
 - Examples:** Current traffic light color, current score of a game, current floor of an elevator, ...
 - Since there can only be a finite number of flip-flops in any machine, the machine only has a finite number of possible states it can be in, hence the name
- Any circuit built from flip-flops is an FSM
 - The counter circuit we just saw is an FSM
 - Even a single flip-flop is an FSM!



State Diagram

- A graphical representation of FSM behavior
 - State: current "status" → the contents of the flip-flops
 - Each possible state is represented by a circle
 - ~~N flip-flops can represent 2^N different states~~
 - State circles also indicate the output(s) in that state
 - Sometimes the output is equal to the state (i.e. the counter)
 - State transitions
 - Represented by an arrow from one state circle to another
 - Labeled with the input condition that causes the FSM to make that transition

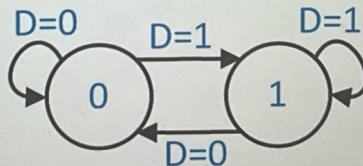


State Diagram of a Flip-Flop

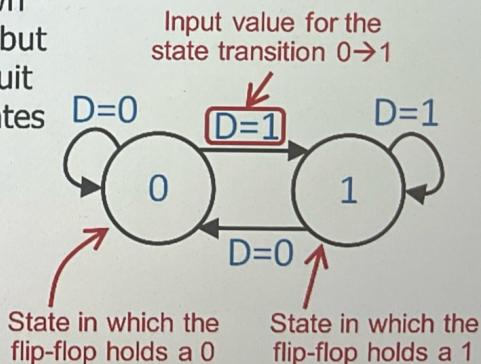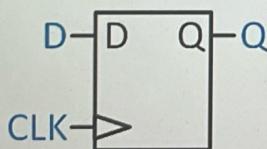- A single flip-flop has 2 states (0 and 1)
- The flip-flop has a single input **D**
- The flip-flop transitions between states at the triggering clock edge based on the value of **D**
 - The clock is NOT shown on the state diagram, but governs when the circuit can move between states



Counter State Diagram

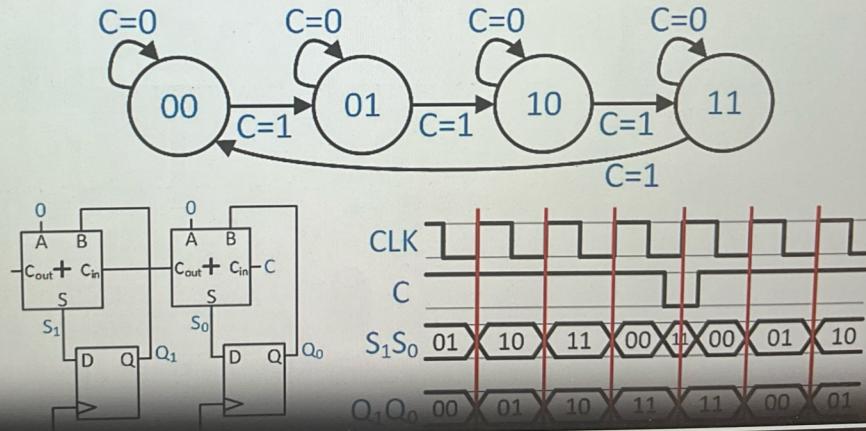- Four states (one per counter value)
 - Transition back to the same state if $C=0$
 - Transition to the state for the next count value if $C=1$



Finite State Machines

The FSM's behavior depends both upon the current state and the input(s)

- The next state is a function of the current state and current input values
- In this class, the output is a function only of the current state


FSM contains combinational
circuits to compute these

(★ Normally, the state has a beginning to
start — Labeled with "Reset")



Common Shorthand Notation

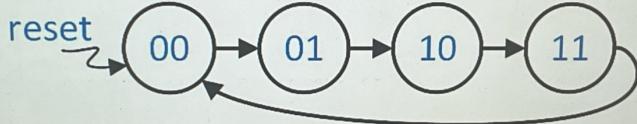
- Some state machines do not have an input, or the input does not affect a particular state transition
 - Example:** a 2-bit counter that always counts





- There is no input that controls what happens here
- At each triggering clock edge, the circuit transitions to the next state (which represents the next count value)
- This type of transition—one not influenced by the input value(s)—is an unconditional transition

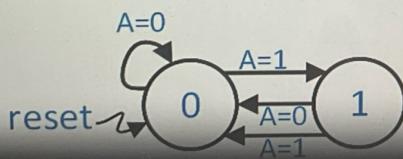Example: Shorthand Notation

- A two-state FSM
- It starts in State 0
- If $A=1$ in State 0, it goes to State 1...
- ...for one cycle before returning to State 0 (regardless of A)
- [if $A=0$ in State 0, it stays in State 0]



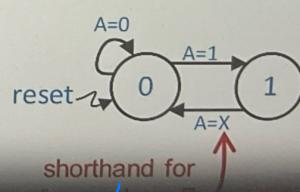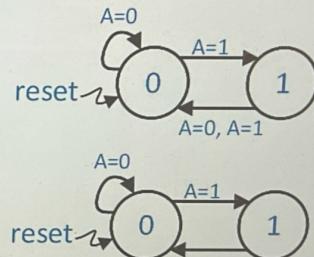- All of the below diagrams are equivalent to the first




shorthand for

"Any value of"

How Do We Implement FSMs?

- Implementing an FSM involves several steps
 - Include flip-flops needed to store the state
 - Design the logic that computes the next state based on the current state and the inputs of the circuit
 - Design the logic that computes the output based on the current state

These are combinational circuits!

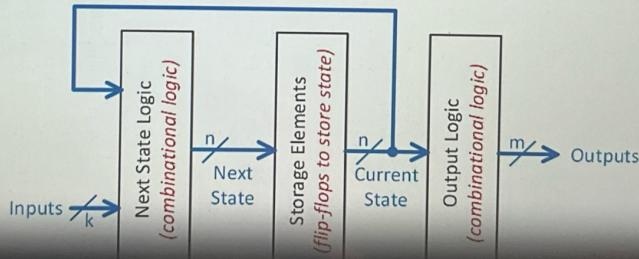

State Table

- Just like we use a **truth table** to characterize a **combinational** circuit, we use a **state table** to characterize a **sequential** circuit
 - Example:


The output (we will name it Y)
is equal to the state

We will name the
current state signal S

State Table


Current State S	Input	Next State S_{NEXT}	Output
	A		Y
0	0	0	0
0	1	1	0
1	0	0	1
1	1	0	1

State Diagram

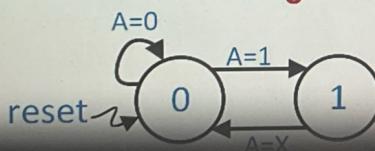

FSM Hardware

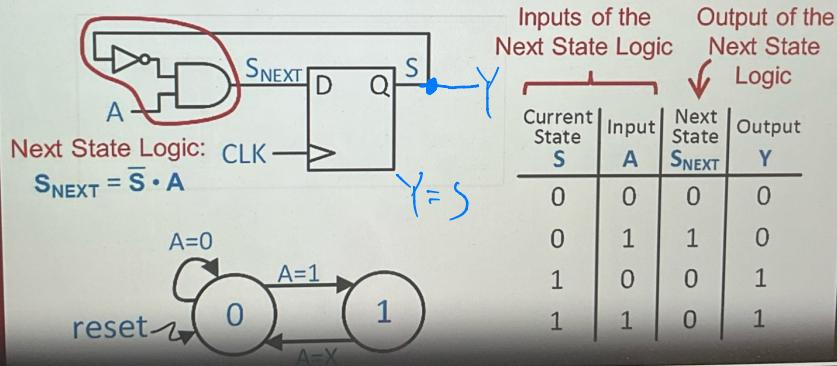
- What does the circuit look like?
- How do we use the state table to design it?




Registers and Memory

Registers

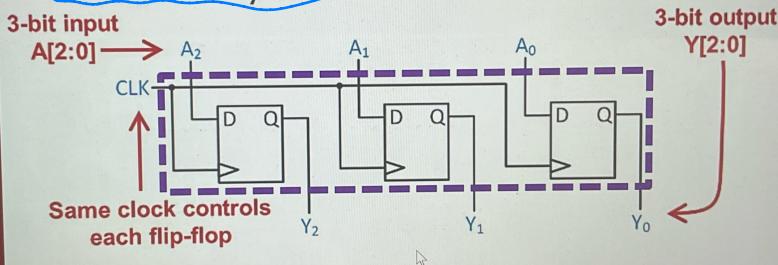- A register is a group of flip-flops used to store multi-bit binary values




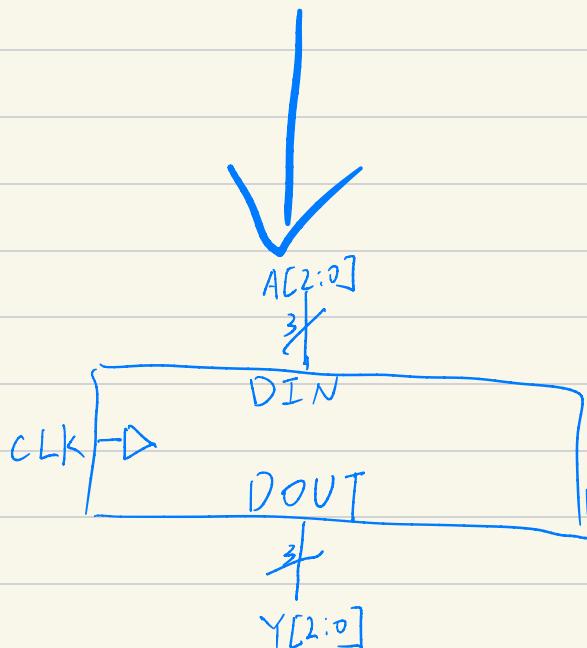- We usually do not show each flip-flop in a register...




Example: Multi-Bit Counters

- 2-bit counter

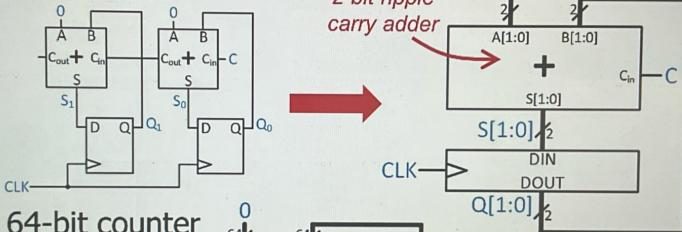




- 64-bit counter

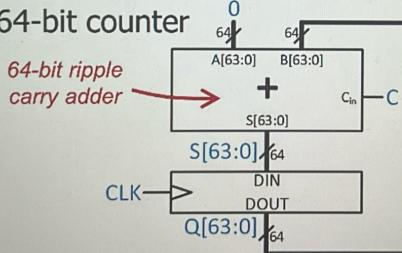

Enable

- Sometimes we want a flip-flop to "hold" its value for multiple clock cycles, regardless of its input
 - But a flip-flop **always** stores the input value at the triggering edge of the clock...
- Solution: add logic so that we can choose to store a new value or the value already in the flip-flop
 - Selection based on the value of a special input signal called an **enable**


EN=1 → choose D
EN=0 → choose Q

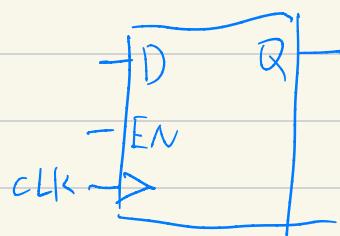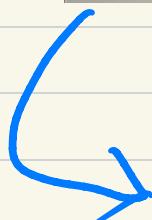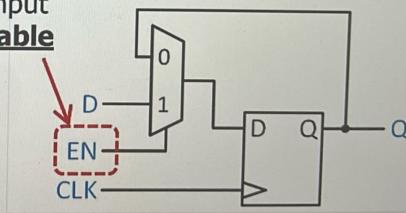

(Flip-Flop with
EN)


Register With Enable

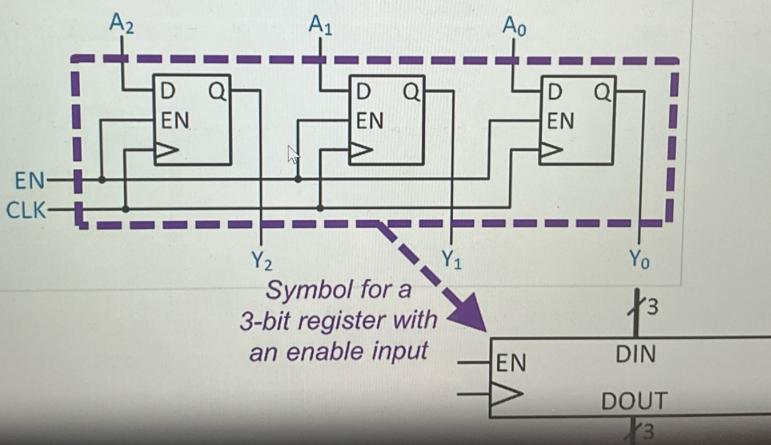- We can also add “enable” capability to registers
 - Every flip-flop in the register shares a common enable




Memory Concepts

- A memory has locations where data is stored
- Each location has a unique address
 - An M-bit number that specifies which of the 2^M locations to access
- Each location stores a single N-bit word
 - N is the data size of the memory (# bits per location)
- The capacity of a memory is the total number of bits that it stores: $(\# \text{ locations}) \times (\text{data size}) = 2^M \times N$
- Only one location can be accessed at a time, either to write (store) a value or read a value
 - A write enable signal (**WE**) controls read vs. write

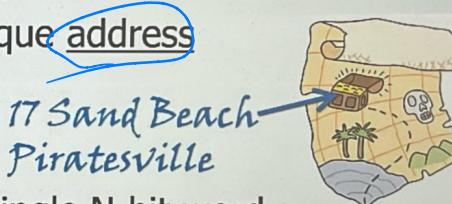



A Logical View of Memory

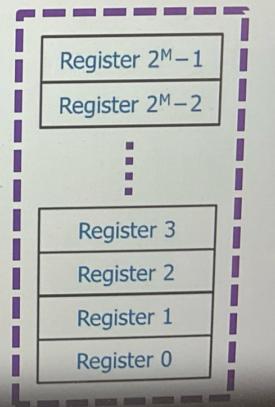- A memory is conceptually like an array of registers
- To access a register, we index into the array using the address for that register
- To write a value, we supply the data to be stored and the address of the location
 - Also, set **WE** to 1 for a write..
- To read a value, we supply the address of the location
 - Also, set **WE** to 0 for a read...
(i.e., do not write)



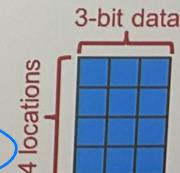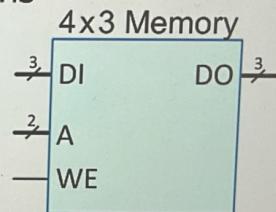Example Memory


- Design first as a “black box”
 - Just the symbol—no inner details are shown
- Build a memory with four locations and a 3-bit data word size
 - Four locations:
 - 2-bit address $\rightarrow A[1:0]$
 - 3-bit data:
 - Data in must be 3 bits $\rightarrow DI[2:0]$
 - Data out must be 3 bits $\rightarrow DO[2:0]$
 - Need to control read/write:
 - Write enable signal $\rightarrow WE$
- The capacity of this memory is:
$$(\# \text{ locations}) \times (\text{data size}) = 4 \times 3 = 12 \text{ bits}$$




$$2^2 \times 3 = 12$$

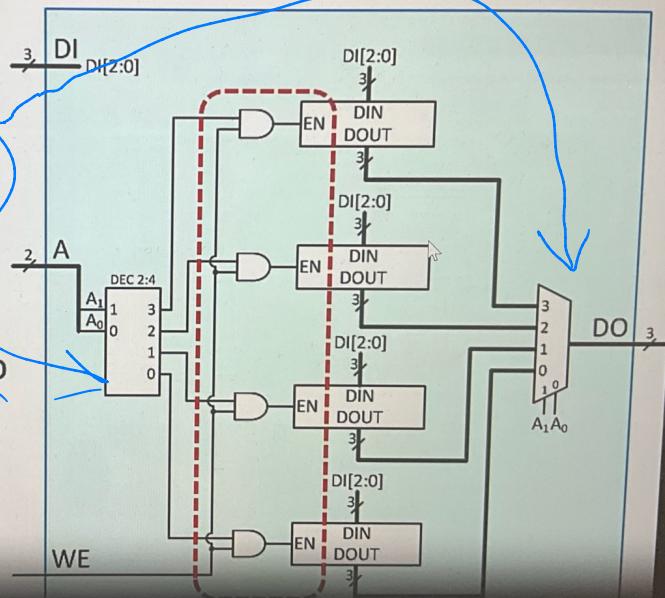Example Memory

- Use four 3-bit registers
 - Clock not shown
- Address selects which register supplies data out
- Address selects which register may be written to
- Selected register will **only** be written if WE=1



Example: Memory Read

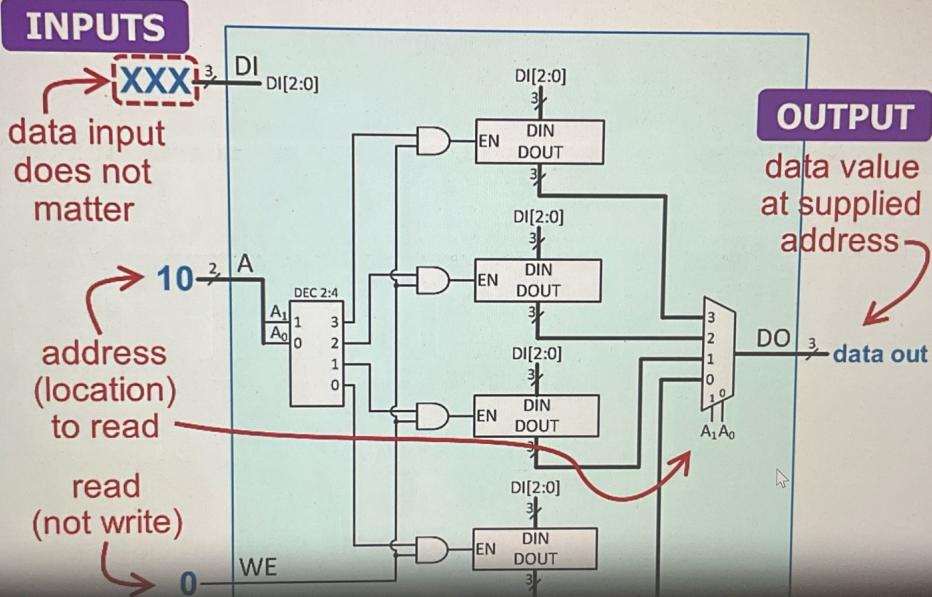


Example: Memory Write

INPUTS

101 → DI
data to be written

00 → A
address (location) to write

1 → WE
write enable

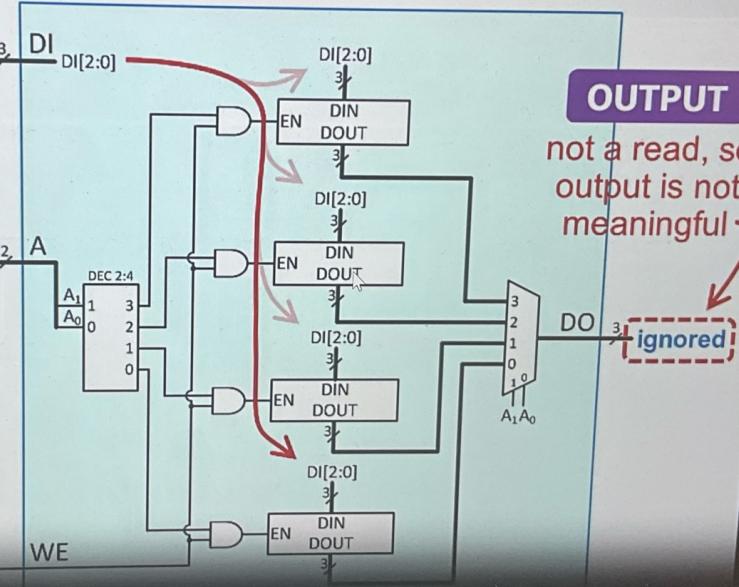

OUTPUT

not a read, so output is not meaningful

ignored