

Logic Circuit From Equation or Truth Table




$$F = ABCD$$

$$F = \overline{A + BC} \cdot D$$

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0


Decoders

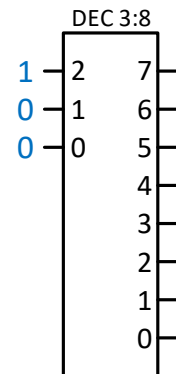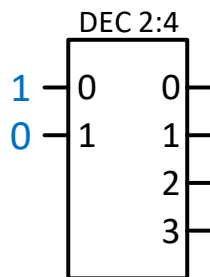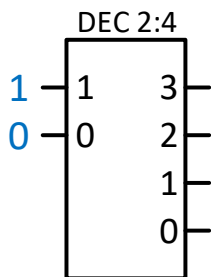
Fill in the output values based on the provided input values.



Decoder Waveform



Complete the decoder waveform.

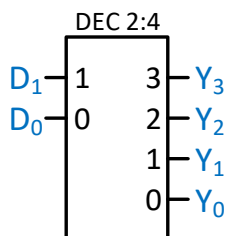

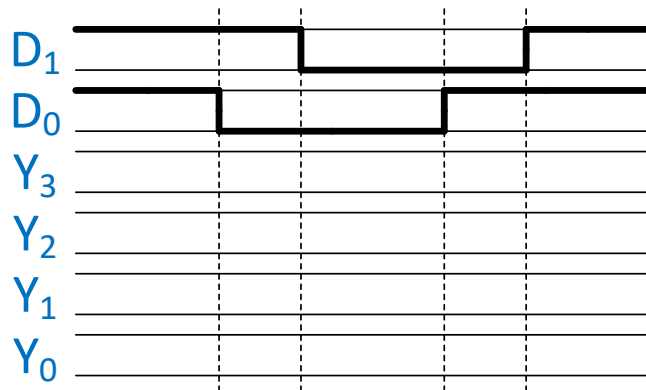



More Decoders

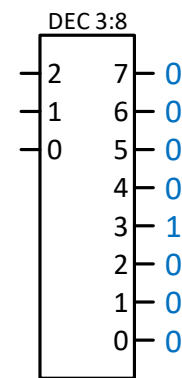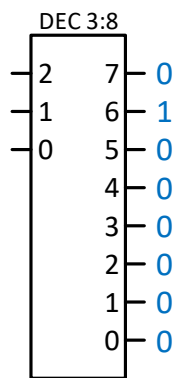Determine what the decoder inputs must be based on the values of the decoder outputs.



Multiplexer Waveform

Complete the multiplexer waveform.

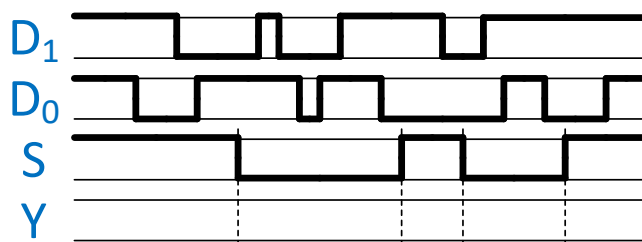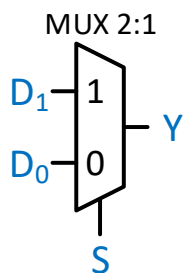

Adders

Connect the adder inputs so that it performs the computation $K + M$, where $K=5$ and $M=6$.

