

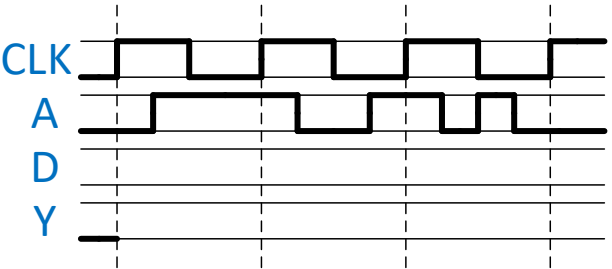


Sequential Circuit Waveform

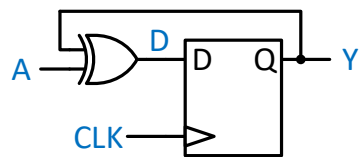

State Machine Analysis

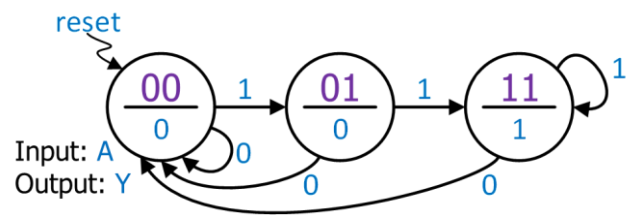


- Input signals?
- Output signals?
- What are the states?
- How many flip-flops?


State Table

CURR STATE	INPUT A	NEXT STATE	OUTPUT Y
0 0	0		
0 0	1		
0 1	0		
0 1	1		
1 0	0		
1 0	1		
1 1	0		
1 1	1		

Waveform

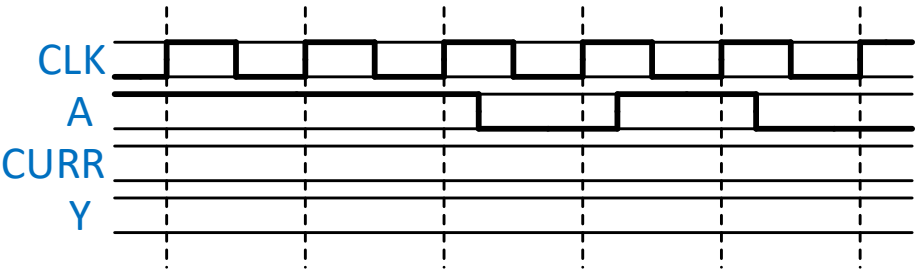

Memory

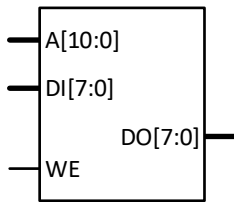

How many address bits?

How do you write to a location?

How many unique address values?

How many locations?

How do you read from a location?

How many bits per location?

What is the word size?

What is the memory's capacity?

FSM Design

Draw a state diagram for an FSM that will flash a light in two repeating sequences, either OFF-**ON**-... or OFF-OFF-OFF-**ON**-... (i.e., $\frac{1}{2}$ or $\frac{1}{4}$ time)


Inputs:

- **FLASH** – flash light if 1, leave light ON constantly otherwise (always finish current flash sequence)
- **SLOW** – flash $\frac{1}{4}$ time if 1, $\frac{1}{2}$ time otherwise (ignore SLOW except when starting a flash sequence)

Output:

- **LIGHT** – light is ON if 1, OFF if 0

Example Waveform

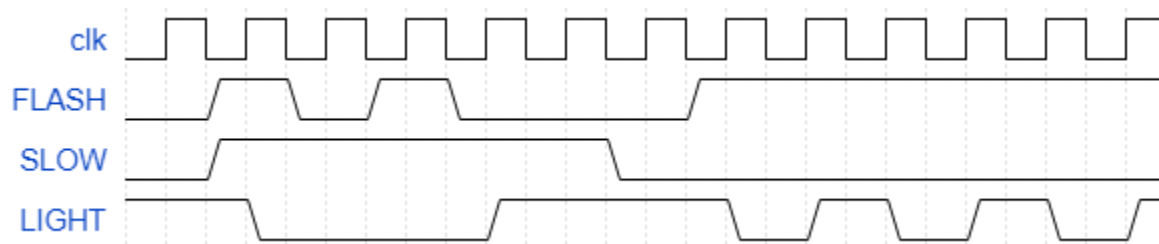

State Diagram