




ECE/CS 252 Intro to Computer Engineering

Week 04 Discussion

1



Logic Gates

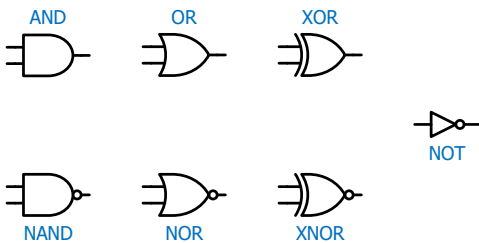

2



Build Logic Circuit From Equation

- $F = ABCD$
- $F = A + \overline{BC} \cdot D$

3



Build Logic Circuit From Truth Table

- Can easily create a functionally correct (but perhaps inefficient) circuit by “reading” truth table
- “When does the output need to equal 1?”


A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

4



Don't Connect Gate Outputs Together!

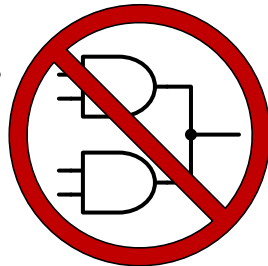- Causes contention!
- What happens if one gate outputs a 1 and the other outputs a 0?




5



Decoders

- What are the output values?

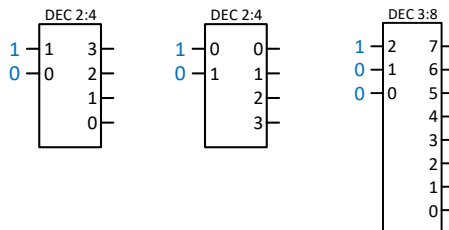


6



Decoder Waveform

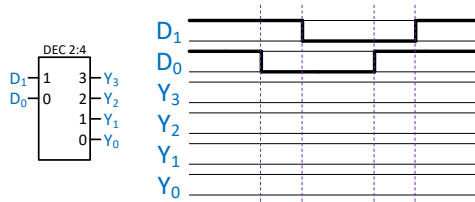
- Complete the waveform for the decoder shown





Decoders


- What must the input values be?

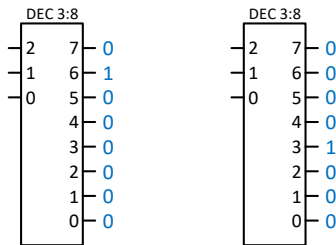



Multiplexer Operation


- Multiplexers make a choice!

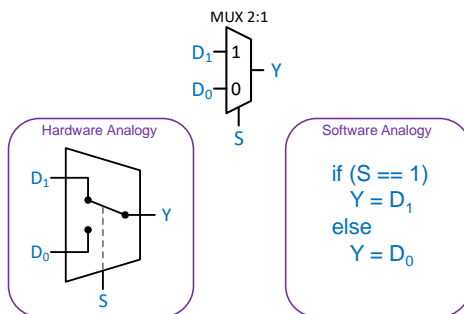



Multiplexer Waveform

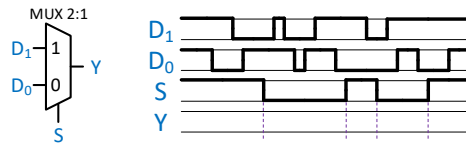- Complete the waveform for the multiplexer shown




10



Adders

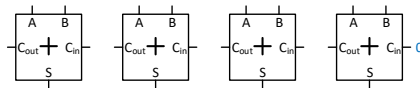- A Full Adder processes **one column** (a single bit position) of a binary addition
- Connect the adder inputs so that it performs the computation $K + M$, where $K=5$ and $M=6$



11



Wrapping Up

- Up Next:
 - Sequential Circuits
 - Flip-Flops
 - Finite State Machines
 - Registers
 - Memory
- Remember the homework!**
- Remember your videos and reading**
 - Including the video quiz!
- Questions?

12