



## ECE/CS 252 Intro to Computer Engineering

### Week 05 Discussion

---

---

---

---

---

---

---



## Sequential Circuits

- Include one or more flip-flops
- Have behavior that depends on more than just the current value of the circuit inputs
  - They need to “remember” some information about past behavior to know how to react to the input
- To “remember”, all of what has happened in the past must be encapsulated into states
  - You know whether you’re happy or sad, but not why...
    - If you need to keep track of why, then you need multiple happy and sad states reflecting the different reasons
- A state is defined by the current value in the flip-flops
  - Since the number of flip-flops must be finite, the number of possible states is also finite, hence the term FSM

---

---

---

---

---


---

---



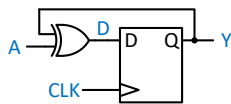
## Sequential Circuit Waveform

- Complete the waveform for the sequential circuit shown at right, assuming signal **Y** is 0 at the start



A	Y	D
0	0	0
0	1	1
1	0	1
1	1	0

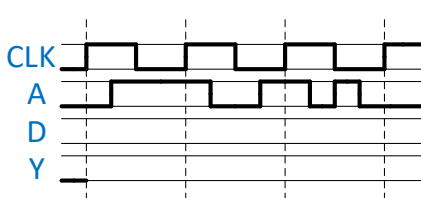

Y	D
0	A
1	A

---

---

---

---


---

---

---



## State Diagram

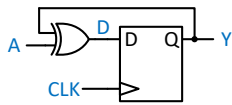

---

---

---

---

---

---


---

---


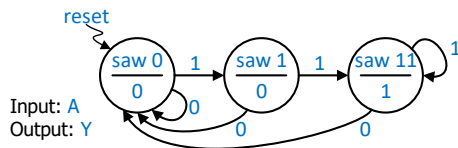
## State Machines

- This state machine detects an input sequence of two 1s in a row
  - It outputs 1 when the two most recent inputs were 1
  - It outputs 0 otherwise



---

---

---

---

---

---


---

---


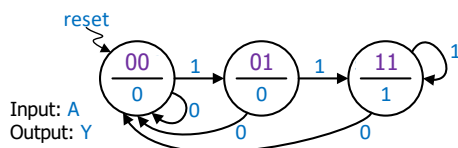
## State Machine Analysis

- Before we do anything else, we'll assign a binary number to each state, such that each is unique
  - This would have to be done before implementing the state machine in hardware, but also makes our analysis easier...



---

---

---

---

---


---

---

---



## State Machine Analysis

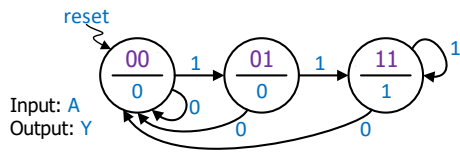

- What is/are the input signal(s)?
- What is/are the output signal(s)?
- What are the states?
- How many flip-flops do we need?

---

---

---

---


---

---

---



## State Machine Analysis

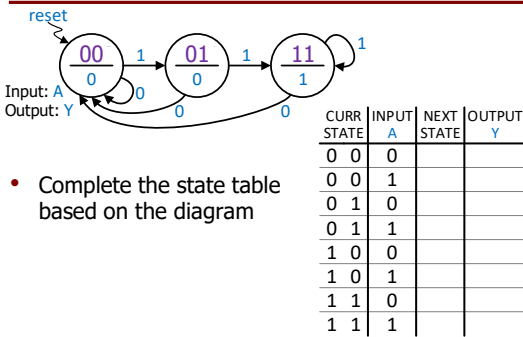

- Complete the state table based on the diagram

---

---

---

---


---

---

---



## State Machine Analysis

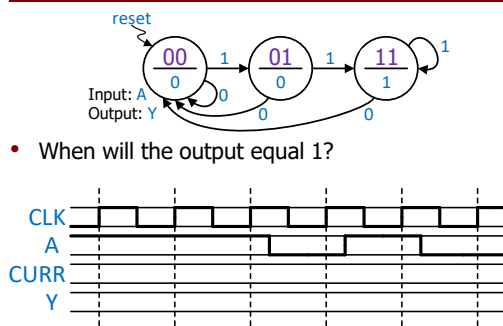

- When will the output equal 1?

- Complete the waveform

---

---

---

---

---


---

---


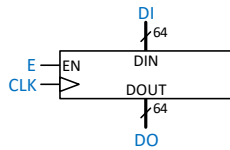
## Registers

- Often want to operate on groups of bits



---

---

---

---

---


---

---

---



## Logical View of Memory

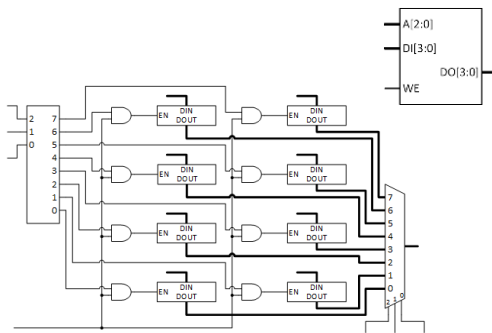

---

---

---

---

---

---


---

---


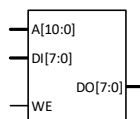
## Memory Parameters

- How many address bits?
- How many unique address values?
- How many locations?
- How many bits per location?
- What is the word size?
- What is the memory's capacity?
- How do you write a location?
- How do you read a location?



---

---

---

---

---

---


---

---


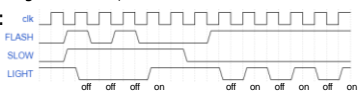
## FSM Design

- Draw a state diagram for an FSM that will flash a light in two repeating sequences, OFF-ON-... or OFF-OFF-OFF-ON-... (i.e.,  $\frac{1}{2}$  or  $\frac{1}{4}$  time)
- Inputs:
  - FLASH – flash light if 1, leave light ON constantly otherwise (always finish current flash sequence)
  - SLOW – flash  $\frac{1}{4}$  time if 1,  $\frac{1}{2}$  time otherwise (ignore SLOW except when starting a flash sequence)
- Output:
  - LIGHT – light is ON if 1, OFF if 0
- Example:



---

---

---

---

---

---

---

---



## State Diagram

- Draw a state diagram for an FSM that will flash a light in two repeating sequences, OFF-ON-... or OFF-OFF-OFF-ON-... (i.e.,  $\frac{1}{2}$  or  $\frac{1}{4}$  time)
- Inputs:
  - FLASH – flash light if 1, leave light ON constantly otherwise (always finish current flash sequence)
  - SLOW – flash  $\frac{1}{4}$  time if 1,  $\frac{1}{2}$  time otherwise (ignore SLOW except when starting a flash sequence)
- Output:
  - LIGHT – light is ON if 1, OFF if 0

---

---

---

---

---

---

---

---



## Wrapping Up

- Up Next:
  - Basic Processor Model
  - von Neumann Compute Model
  - Instruction Processing
- Remember your videos and reading
  - Including the video quiz!
- Questions?

---

---

---

---

---

---

---

---